

Loudspeaker Protection and Muting

© October 1999, Rod Elliott (ESP)
Updated September 2020

Google Bookmarks

Facebook

More 27

Please Note: PCBs are available for the latest revision of this project. Click the image for details.

Introduction

Please note that the PCB version is different from the circuit shown in this article. It is actually simpler, but achieves the same functions. Full details are available when you purchase the board. The latest boards are Revision-A, and are slightly different from the previous version. The basic circuit arrangement is shown in Figure 5.

The P33 PCB can be used with a pair of [Project 198](#) MOSFET relays, which is especially useful if you amplifyer has supply voltage of more than ±50V. At high voltages, the relay contacts will (not might) arc, and if the fault voltage is around 60V or more the relay will be incapable of extinguishing the arc. See [Relay Failure](#) below for graphic evidence of this. I've also run many tests on relays, and a destructive arc is almost guaranteed with a voltage of 60V at 10A or more (assuming a voicecoil resistance of 5.6Ω). A new sub-section has been included to show how to use P198 MOSFET relay boards with P33.

Many hi-fi amplifiers and professional power amps (and loudspeaker systems) provide some of protection, either to protect the speakers from an amp fault, and/or vice versa. Some of these are implemented at a very basic level - for example the use of a 'poly-switch'. The poly-switch is a non-linear resistor, having a low resistance at normal temperatures and a much higher resistance at some designated temperature. Unlike 'ordinary' thermistors whose characteristics are more or less linear, the poly switch has a rapid transition once the limit has been reached.

I don't like poly-switches, because I know that the introduction of a non-linear element is going to add some degree of distortion, and because of a finite resistance, will degrade damping. This (i.e. damping) is usually not an issue IMO, but to many audiophiles it is of prime importance. (I shall not pursue this argument here, however - see [Impedance](#) for more info.)

The basic requirement of a speaker protection circuit requires that any potentially dangerous DC flow to the speakers should be interrupted as quickly as possible. There are a few issues that need to be solved to ensure that this will happen fast enough to stop the loudspeaker drivers from being damaged, and this becomes more critical if a biamped (and even more so with triamped) system is being used.

Naturally, one can simply rely on fuses. Although these also have finite resistance it is small, and use of fast blow fuses can be quite effective. The rating becomes quite critical, and fast blow fuses are essential. The problem with this approach is that if the fuse is of a suitable value to provide good protection, it will be subjected to considerable thermal stress since it is operating at close to its limits. Metal fatigue will create the problem of nuisance blowing, where the fuse blows simply because it is 'tired' of the constant flexing caused by temperature variations. I know this from personal experience with loudspeakers I had many years ago - they used fuses to protect the tweeters. Nuisance fuse failures were common (and a very annoying).

This project explains the principles, and shows a suitable detection method that may be applied. The speed of the relay used is another critical factor, and we shall see that the conventional method of preventing the relay's back-EMF from destroying the drive transistor also slows down the response to a potentially unacceptable degree.

The circuit also includes a mute function, which leaves the speakers disconnected until the amplifier has settled, and disconnects the speakers as quickly as possible after power is removed to prevent the turn-off noises that some amps generate. These can range from a low level thump 5 to 10 seconds after power is turned off, to whistles, squeaks and other strange noises that I have heard from amps over the years.

Please Note: While the circuit shown here and the PCB version can both be made to work just fine with high supply voltages (such as ±50V as might be used with P101 and many other amplifiers), because what the majority of relays will be totally incapable of breaking that voltage and the resulting current under fault conditions. The DC causes a significant arc, and this is more than count on it. While relays capable of breaking perhaps 10A or more at 70V DC are available, they will be expensive and probably hard to get. Unfortunately, there are few options for an alternative method. The relays article does offer some solutions.

If you are lucky, the fuse(s) will blow before the relay is destroyed, but I wouldn't count on it. While relays capable of breaking perhaps 10A or more at 70V DC are available, they will be expensive and probably hard to get. Unfortunately, there are few options for an alternative method. The relays article does offer some solutions.

Using the relays as shown below (with the normally open contact connected to ground), the arc will be diverted from the speaker and will be to ground, but the relay will almost certainly be destroyed unless a specialised component is used. Despite their apparent simplicity, relays are actually rather complex devices. A great deal of engineering goes into the development of the contacts, but operating them in excess of the manufacturer's ratings means that nothing is certain. For more information, see the two-part article about [Relays](#).

Please make sure that you understand the limitations of any such circuit (not just mine - the same applies to all loudspeaker protection circuits). The circuits themselves are not limited, but the relays must certainly be.

MOSFET Relay

If your amplifier has supply voltage above ±35V, you may want to consider using [Project 198](#) MOSFET relays. You simply wire up a couple of the PCBs with MOSFETs suitable for your requirements, plus the IC and a few other parts. With the optimum choice of MOSFETs, disconnecting an amplifier with ±100V DC supplies is not a problem - that's a 600W/ 8Ω (1.2kW/ 4Ω) amplifier, and there can be no arc because the switching is done with MOSFETs, not electromechanical contacts.

For a stereo amp, you'll need two P198 boards (and can no one else has *anything* that comes close), and you only need about 10mA to drive them. The two input sections are simply wired in series with a limiting resistor to suit the P33 board's supply voltage. The MOSFET relay is perfectly suited to any amplifier voltages you'll encounter, and it's fully isolated so there can be no unwanted interactions.

If you use MOSFETs with an 'on' resistance ($R_{DS(on)}$) of less than 10mΩ, the average dissipation will be less than 1W each, even at an output current of 10A RMS (a power of 400W/ 4Ω continuous - highly unlikely with any normal programme material). This is a new PCB from the ESP line-up, and it's the only one of its type that you can buy. It's specifically designed for AC - most of those you can buy are DC only, and the few AC versions available have very slow turn-on and may be unable to support high current. If there's enough interest I'll be able to get more made and reduce the price.

Why DC Kilns Speakers

There are innumerable misconceptions as to what happens to a loudspeaker drive when it's subjected to DC. Small levels of DC (less than 1V) usually do no more than displace the cone slightly, and it's generally accepted that ±100mV is the maximum that should occur. This represents a power of 2.5mW into a 4Ω load. A 100W/ 8Ω amplifier will typically use ±42V supplies, although some will use up to ±56V DC.

When the amp is providing its maximum power, the output voltage is 28V RMS, assuming a steady tone. We don't listen to steady tones (especially at 100W!), and music has a dynamic range of around 10dB (although some has less - 5dB is the minimum generally achievable). We'll stay with 10dB, meaning that the average power from the magnet gap and because it's not moving there is no effective cooling. The voicecoil will reach a dangerous temperature in a few seconds, and if the DC isn't disconnected quickly, the speaker will fail. This is called catching on fire!

The answer is a DC detector with a relay, which will disconnect the DC fault current. This will be in the order of 7A, which is more than sufficient to cause almost *all* miniature relays to sustain a continuous arc. If the speaker isn't shorted by the relay, the arc current will be in the order of 4A or more directly to the speaker (arcs have impedance, but it's highly variable). With a sustained power of somewhere between 100W and 250W and no cone movement, very few speakers will survive.

The vast majority of published circuits do not show the relay shorting the speaker, and protection is only afforded with DC voltages of 35V or less. Higher powered amplifiers are far worse, and there is no common relay that can break a 70V DC arc at a current of more than a few hundred millamps at most. More than twenty years have passed since the design shown here was published, and almost no-one else has updated their flawed circuits. To be able to break a 70V DC arc at any likely current requires a relay with at least 1.6mm of contact clearance - this is extremely uncommon!

The Circuit

It is important to identify the lowest frequency likely to be passed to a speaker, because this determines the delay that must be introduced to prevent low frequencies from triggering the protection circuit (nuisance tripping). For practical purposes, a frequency limit of 20Hz is satisfactory for a full range system, and this means that a minimum 25ms delay is essential. In reality, due to the combination of low frequencies, and asymmetrical waveforms at higher frequencies, a greater delay will normally be required. Unfortunately, the greater the delay, the greater the risk of drivers being damaged. In a full range system (i.e. using passive crossovers), midrange and tweeters will be offered some protection by the capacitors used in the crossover network, but these are missing in a biamped or triamped system. For this reason, it is important that the circuit can be easily modified to change the initial time delay before the system detects the DC and disconnects the speakers.

Be aware that you will need to use higher voltage transistors throughout if the amplifier is operated at more than ±60V. The transistors shown are rated for 65V, but using any transistor close to its voltage limit is unwise. Provided you understand the circuit and know what you are doing, it's simple enough to run the circuit from a lower voltage if it's available. Alternatively, a simpler zener regulated supply can be created to power the circuit itself (but not the relays, as they draw too much current). Relay selection becomes a lot for high voltage supplies!

