

Soft-Start Circuit For Power Amps (Inrush Current Limiter)

© December 1999, Rod Elliott (ESP)
Updated October 2020



Please Note: PCBs are available for the latest revision of this project. Click the PCB image for details.

WARNING: This circuit requires experience with mains wiring. Do not attempt construction unless experienced and capable. Death or serious injury may result from incorrect wiring.

Updates ...

PCBs are available for a somewhat modified version of the soft-start project, otherwise known as an inrush current limiter. Rather than the MOSFET switch, the PCB version uses a cheap amp, and provides power and soft start switching. Full details are available when you purchase the PCB, but the schematic and a brief description is shown below. There's also a photo of the board a little further down this page.

The delay time for all circuits shown has been revised. The optimum is around 100ms - sufficient for around 5 full cycles at 50Hz, or 6 cycles at 60Hz. It is also quite alright to run the transformer to around 200-600% of full load current at start-up, and the formulae have been revised for up to 200%. Without the soft-start, inrush current can be so high as to be limited only by wiring resistance - varied in excess of 50A is not at all uncommon for average sized 230V transformers.

The main timing resistor (R1) may need to be changed to get the required delay. MOSFETs have a wide variation of gate threshold voltage, and the timing will need to be adjusted to suit the MOSFET you have in your circuit (assuming you wish to use one of the circuits shown below).

It's worth pointing out that there are many soft start circuits published (and foremost people have copied the text from the introduction below), and quite a few are available (and not-so-notice) to determine the proper value and size, and manufacturers don't help much. The specification format from one maker rarely matches that of another, and making things is rarely easy. Some quote a maximum current, others a rating in Joules, and some include almost nothing except the nominal resistance at 25°C and the dimensions - hardly helpful.

Many people like the idea of using NTC (negative temperature coefficient) thermistors for inrush limiting, with a common claim being that no additional circuitry is needed. In a word *DO NOT*. This may be controversial, but I have personally seen (yes, with my very own eyes) NTC thermistors explode mightily if there is a fault. Resistors can also fail, but the failure is (usually) contained - there are exceptions of course. In general, NTC thermistors are designed for very high peak current, but as noted earlier, you will see wildly different ways to describe the same thing, with almost no commonality between makers.

If the relay fails to operate because you didn't listen to me and used the amp's supply, the thermistor will (in theory) become a low resistance due to the current flow and the fuse will blow. However, if current is too high due to a major fault, the thermistor may explode before the fuse has a chance. I'm unsure why some people insist that the thermistor is somehow 'better' than resistors - it isn't, and in some cases may even be a less robust solution. As noted below, a resistor (or thermistor) value of about 50 ohms (230V) or 25 ohms (120V) is a pretty good overall compromise, and works perfectly with transformers up to about 500VA. The resistance should be reduced for higher power transformers.

If a thermistor is used, it needs to be sized appropriately. While some small thermistors may appear quite satisfactory, they will often be incapable of handling the maximum peak current. I suggest that you read the article on [inrush protection circuits](#) for more information. A suitably rated thermistor can be used in any version of this project (including the PCB based unit shown in Figure 6).

Under no circumstances will I ever suggest a thermistor without a bypass relay for power amplifiers, because their standby or low power current is generally insufficient to get the thermistor hot enough to reduce the resistance to a sensible value. You will therefore get power supply voltage modulation, with the thermistor constantly thermally cycling. This typically leads to reduced life for the thermistor, because the thermal cycling is the equivalent of an accelerated lifetime test regime (that's basically one of the tests that is done in the manufacturer's lab to find out how long they will last in use).

If there is enough continuous current (Class-A amplifier for example), the surface temperature of any fully functioning thermistor is typically well over 100°C, so I consider bypassing mandatory to prevent excess unwanted heat. A bypass circuit also means that the thermistor is ready to protect against inrush current immediately after power is turned off. Without the bypass, you may have to wait 30 seconds or more before it has cooled.

Thermistors - Important !

Using thermistors rather than resistors is a common question, and while there are many caveats they will generally work well. Unfortunately, it can be very difficult for the novice (and not-so-notice) to determine the proper value and size, and manufacturers don't help much. The specification format from one maker rarely matches that of another, and making things is rarely easy. Some quote a maximum current, others a rating in Joules, and some include almost nothing except the nominal resistance at 25°C and the dimensions - hardly helpful.

Many people like the idea of using NTC (negative temperature coefficient) thermistors for inrush limiting, with a common claim being that no additional circuitry is needed. In a word *DO NOT*. This may be controversial, but I have personally seen (yes, with my very own eyes) NTC thermistors explode mightily if there is a fault. Resistors can also fail, but the failure is (usually) contained - there are exceptions of course. In general, NTC thermistors are designed for very high peak current, but as noted earlier, you will see wildly different ways to describe the same thing, with almost no commonality between makers.

If the relay fails to operate because you didn't listen to me and used the amp's supply, the thermistor will (in theory) become a low resistance due to the current flow and the fuse will blow. However, if current is too high due to a major fault, the thermistor may explode before the fuse has a chance. I'm unsure why some people insist that the thermistor is somehow 'better' than resistors - it isn't, and in some cases may even be a less robust solution. As noted below, a resistor (or thermistor) value of about 50 ohms (230V) or 25 ohms (120V) is a pretty good overall compromise, and works perfectly with transformers up to about 500VA. The resistance should be reduced for higher power transformers.

If a thermistor is used, it needs to be sized appropriately. While some small thermistors may appear quite satisfactory, they will often be incapable of handling the maximum peak current. I suggest that you read the article on [inrush protection circuits](#) for more information. A suitably rated thermistor can be used in any version of this project (including the PCB based unit shown in Figure 6).

Under no circumstances will I ever suggest a thermistor without a bypass relay for power amplifiers, because their standby or low power current is generally insufficient to get the thermistor hot enough to reduce the resistance to a sensible value. You will therefore get power supply voltage modulation, with the thermistor constantly thermally cycling. This typically leads to reduced life for the thermistor, because the thermal cycling is the equivalent of an accelerated lifetime test regime (that's basically one of the tests that is done in the manufacturer's lab to find out how long they will last in use).

If there is enough continuous current (Class-A amplifier for example), the surface temperature of any fully functioning thermistor is typically well over 100°C, so I consider bypassing mandatory to prevent excess unwanted heat. A bypass circuit also means that the thermistor is ready to protect against inrush current immediately after power is turned off. Without the bypass, you may have to wait 30 seconds or more before it has cooled.

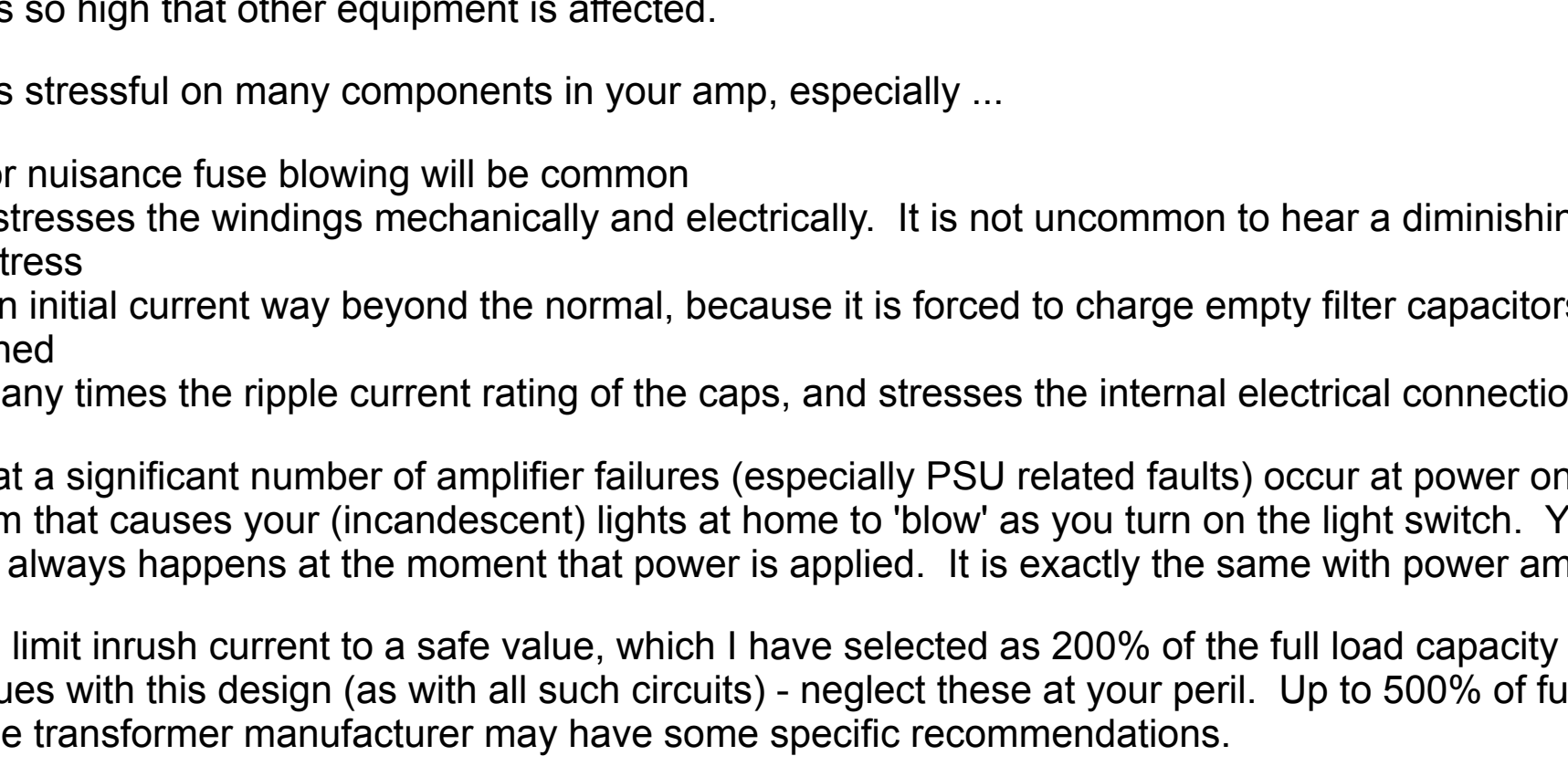


Photo Of Soft-Start PCB Using Thermistors

The photo above serves two purposes. It shows a completed P39 board, and includes suitable thermistors showing how they mount to the PCB, which needs an extra hole to wire the thermistors in series - this is easily drilled by the constructor. There are two 10 ohm thermistors, wired in series to give a total of 20 ohms. The relay bypasses the thermistors after around 100ms when power is applied, and this reduces the worst case inrush current to around 10A with 230V input. The total resistance includes the primary resistance of the transformer (3 ohms has been assumed in the calculation).

Introduction

When your monster (or not so monster) power amplifier is switched on, the initial current drawn from the mains is many times that even at full power. There are two main reasons for this, as follows ...

- Transformers will draw a very heavy current at switch on, until the magnetic flux has stabilised. (The effect is worst when power is applied as the AC voltage passes through zero, and is minimised if power is applied at the peak of the AC waveform. This is exactly the opposite to what you might expect.)
- At power on, the filter capacitors are completely discharged, and act as a short circuit for a brief (but possibly destructive) period

These phenomena are well known to manufacturers of very high power amps used in PA and industrial applications, but 'soft start' circuits are not commonly used in consumer equipment. Anyone who has a large power amp - especially one that uses a toroidal transformer - will have noticed a momentary dimming of the lights when the amp is powered up. The current drawn is so high that other equipment is affected.

This high inrush current (as it is known) is stressful on many components in your amp, especially ...

- Fuses - these must be slow-blow, or nuisance fuse blowings will be common
- Transformer - the massive current stresses the windings mechanically and electrically. It is not uncommon to hear a diminishing mechanical buzz as the chassis and transformer react to the magnetic stress
- Bridge rectifier - this must handle the initial current way beyond the normal, because it is forced to charge empty filter capacitors - these look like a short circuit until a respectable voltage has been reached
- Capacitors - the inrush current is many times the ripple current rating of the caps, and stresses the internal electrical connections

It should come as no surprise to learn that a significant number of amplifier failures (especially PSU related faults) occur at power on (unless the operator does something foolish). This is exactly the same problem that causes your (incandescent) lights at home to 'blow' as you turn on the light switch. You rarely see a light bulb fail while you are quietly sitting there reading, it almost always happens at the moment that power is applied. It is exactly the same with power amplifiers.

The circuit presented here is designed to limit inrush current to a safe value, which I have selected as 200% of the full load capacity of the power amplifier. Please be aware that there are important safety issues with this design (as with all such circuits) - neglect these at your peril. Up to 500% of full power is quite alright, and the decision as to which value to use is up to you. The transformer manufacturer may have some specific recommendations.

NOTE: If you are unwilling to experiment, the relay operation must be 100% reliable, your mains wiring must be to an excellent standard, and some metalwork may be needed. There is nothing trivial about this circuit (or any other circuit designed for the same purpose), despite its apparent simplicity.

Transformer Characteristics

It can be helpful to know the basics of your transformer, especially the winding resistance. From this, you can work out the worst case inrush current. This table is shown in [Transformers, Part 2](#) and is abridged here. Transformers with a winding resistance of more than 10 ohms (230V types) don't need a soft start circuit. Although the peak current can reach around 30A, that's well within the abilities of a slow blow fuse and normally never causes a problem. Of course, if you want to use a soft start on smaller transformers, there's no reason not to, but above the added cost.

VA	Reg %	R _{EQ} - 230V	R _{EQ} - 120V	Diameter	Height	Mass (kg)
160	9	10 - 13	2.9 - 3.4	105	42	1.50
225	8	6.9 - 8.1	1.9 - 2.2	112	47	1.90
300	7	4.6 - 5.4	1.3 - 1.5	115	58	2.25
500	6	2.4 - 2.8	0.65 - 0.77	136	60	3.50
625	5	1.6 - 1.9	0.44 - 0.52	142	68	4.30
800	5	1.3 - 1.5	0.35 - 0.41	162	60	5.10
1000	5	1.0 - 1.2	0.28 - 0.33	165	70	6.50

Table 1 - Typical Toroidal Transformer Specifications

The maximum inrush current is roughly the mains voltage divided by the winding resistance. There's a lot more detail info on this (including oscilloscope captures) in the [Inrush Current](#) article. It also includes waveforms with a rectifier followed by a large capacitance and a load, and will help you to understand the need for protection circuits with large transformers.

Description

Although the soft start circuit can be added to any sized transformer, the winding resistance of 300VA and smaller transformers is generally sufficient to prevent a massive surge current. Use of a soft start circuit is definitely recommended for 500VA and larger transformers.

The worst case instantaneous current is limited only by the transformer's primary winding resistance and the effective resistance of the incoming mains supply (typically less than 1 ohm). For a 500VA transformer at 230V this will be in the order of 2.5 to 3 ohms, so the worst case current could easily exceed 70 amps. Even a slow-blow fuse is stressed by such a current surge, and that's why I am so adamant that soft-start is a really good idea.

As an example, a 500VA transformer is fairly typical of many high power domestic systems. Assuming an ideal load (which the rectifier is not, but that's another story), the current drawn from the mains at full power is ...

$$I = VA / V \quad (1) \text{ Where VA is the VA rating of the transformer, and V is the mains voltage used}$$

Since I live in a 230V supply country I will use this for my calculations, but they are easy for anyone to do. Using equation 1, we will get the following full power current rating from the mains (neglecting the transformer winding resistance) ...

$$I = 500 / 230 = 2.2A \quad (\text{close enough})$$

At a limit of 200% of full power current, this is 4.4A AC. The effective resistance is easily calculated using Ohm's law ...

$$R = V / I \quad (2) \\ R = 230 / 4.4 = 52 \text{ Ohms (close enough)}$$

Not really a standard value, but 3 x 150 Ohm 5W resistors in parallel will do just fine, giving a combined resistance of 50 Ohms. A single 47 ohm or 56 ohm resistor could be used, but the power and/or over 900W (instantaneous) is a little daunting. We don't need anything like that for normal use, but be aware that this will be the dissipation under certain fault conditions.

To determine the power rating for the ballast resistor, which is 200% of the transformer power rating at full power ...

$$P = V^2 / R \quad (3)$$

For this resistance, this would seem to indicate that a 930W resistor is needed (based on the calculated 50 Ohms), a large and expensive component indeed.

In reality, we need no such thing, since the resistor will be in circuit for a brief period - typically around 100-150ms, and the amp will (hopefully) not be expected to supply significant output power until stabilised. The absolute maximum current will only flow for 1 half-cycle, and diminishes rapidly after that.

The only thing we need to be careful about is to ensure that the ballast resistor is capable of handling the inrush current. During testing, I managed to split a ceramic resistor in half because it could not take the current - this effect is sometimes referred to as 'Chenobyling', after the nuclear disaster in the USSR some years ago, and is best avoided. ☹

It is common for large professional power amps to use a 50W resistor, usually the chassis mounted aluminium bodied types, but these are expensive and not easy for most constructors to get. For the above example, 3 x 5W ceramic resistors in parallel (each resistor being between 150 and 180 Ohms) will give us what we want, and is a reasonable compromise.

For US (and readers in other 120V countries), the optimum resistance works out to be 12 Ohms, so 3 x 33 Ohm 5W resistors should work fine (this gives 11 Ohms - close enough for this type of circuit).

It has been claimed that the resistance should normally be between 10 and 50 ohms, and that higher values should not be used. I shall leave this to the reader to decide, since there are (IMO) good arguments for both ideas. As always, this is a compromise situation, and different situations call for different approaches.

A 10 ohm resistor is the absolute minimum I would use, and the resistor needs to be selected with care. The surge current is likely to demolish lesser resistors, especially with a 230V supply. While it is true that as resistance is reduced, the resistance wire is thicker and more tolerant of overload, worst case instantaneous current with 10 ohms is 22A at 230V. This is an instantaneous dissipation of 5.200W (ignoring other resistances in the circuit), and it will cause an extremely robust resistor to withstand this even for short periods. For 120V operation, the peak current will only be 12A, reducing the peak dissipation to 1.440W.

In reality, the worst case peak current will never be reached, since there is the transformer winding resistance and mains impedance to be taken into account. On this basis, a reasonable compromise limiting resistor (and the values that I use) will be in the order of 50 Ohms for 230V (3 x 150 ohm 5W), or 11 Ohms (3 x 33 ohm 5W) for 120V operation. Resistors are wired in parallel. You may decide to use these values rather than calculate the value from the equations above, and it will be found that this will work very well in nearly all cases, but will still allow the fuse to blow in case of a fault. These values are suitable for transformers up to 500VA.

This is in contrast to the use of higher values, where the fuse will (in all probability) not blow until the relay closes. Although the time period is short, the resistors will get very hot, very quickly. Thermistors may be helpful, because they get hot their resistance falls, and if suitably rated they will simply fall to a low enough resistance to cause the fuse to blow.

Another good reason to use a lower value is that some amplifiers have a turn-on behaviour that may cause a relatively heavy current to be drawn for a brief period. These amplifiers may not reach a stable operating point with a high value resistance in series, and may therefore cause a heavy speaker current to flow until full voltage is applied. This is a potentially disastrous situation, and must be avoided at all costs. If your amplifier exhibits this behaviour, then the lower value limiting resistors *must* be used.

If flaky mains are a 'feature' where you live, then I would suggest that you may need to set up a system where the amplifier is switched off if the mains fails for more than a few cycles at a time. The AC supply to a toroidal transformer only has to 'go missing' for a few cycles to cause a substantial inrush current, so care is needed.

If a thermistor is used, I suggest a robust version, rated for a nice high maximum current. 20mm diameter devices are generally rated for much higher currents than they are likely to need, so will suffer minimal thermal cycling. A common round value is 10 ohms at 25°C - this does mean higher peak currents than I suggest above, but you can always use two in series - especially for 230V operation.

Bypass Circuit

Many of the large professional amps use a TRIAC (bilateral silicon controlled rectifier), but I use a relay for a number of very good reasons ...

- Relays are virtually indestructible
- They are easy to obtain almost anywhere
- Useful isolation is provided, so control circuitry is not at mains potential
- No RF noise or other spurious emissions from the relay, but these are low level, but can be very troublesome to eliminate from TRIAC circuits
- No heatsink is needed, eliminating a potential safety hazard should there be an insulation breakdown between TRIAC and heatsink

They will also cause their share of problems, but these are addressed in this project. The worst is providing a suitable coil voltage, allowing commonly available devices to be used in power amps of all sizes and power voltages.

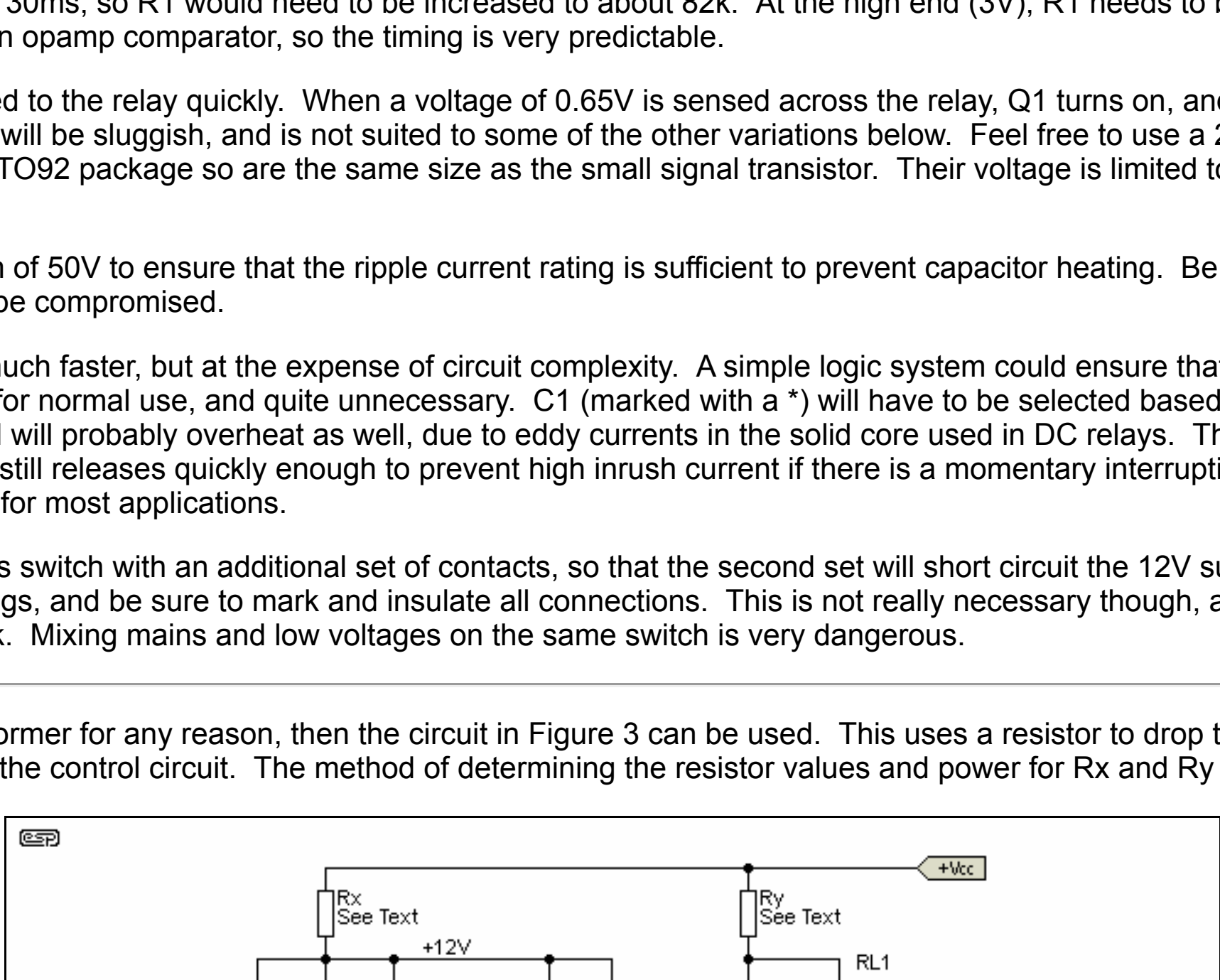


Figure 1 - Soft-Start Resistors and Relay Contacts

Figure 1 shows how the resistors are connected in series with the supply to the transformer, with the relay contacts short circuiting the resistors when the relay is activated. This circuitry is all at the mains voltage, and must be treated with great respect.

'A' represents the Active (Live or Hot) lead from the mains switch, and 'SA' is the 'soft' Active, and connects to the main power transformer. Do not disconnect or bypass any existing wiring, simply place the resistor pack in series with the existing transformer!

Do not attempt any wiring unless the mains lead is disconnected, and all connections must be made so that accidental contact to finger or chassis is not possible under any circumstances. The resistors must be mounted using an aluminium bracket (see above) to ensure that the resistors are well separated from each other, and to provide a safe distance from the chassis and shroud - where this seems impossible, use insulation to prevent any possibility of contact. Construction notes are shown later in this project. The safety aspect of this project cannot be stressed highly enough!

The relay contacts must be rated for the full mains voltage, and at least the full power current of the amplifier. The use of a relay with at least 10A contact rating is strongly recommended.

HINT: You can also add a second relay to move the input until full power is applied. I shall leave it to you to make the necessary adjustments. You will have to add the current for the two relays together, or use separate supply feeds if utilising the existing internal power supply voltage.

Control Circuits

If a 12V supply were to be available in all power amps, this would be very simple, but unfortunately this is rarely the case. Most amps will have DC supplies ranging from +/-25V to about +/-70V, and any attempt to obtain relays for these voltages will be met with failure in the majority of cases.

An auxiliary supply can be added, but this means the addition of a second transformer, which may be quite impossible due to space limitations in some cases. It is still a viable option (and is the safest way to go), and a control circuit using this approach is shown in Figure 2. This is the simplest to implement, but may not consider the added cost of the second transformer hard to justify. IMO it's not an issue, and is by far the preferred option. It's pretty much mandatory for Class-A amps (See [Class-A Amplifiers](#)).

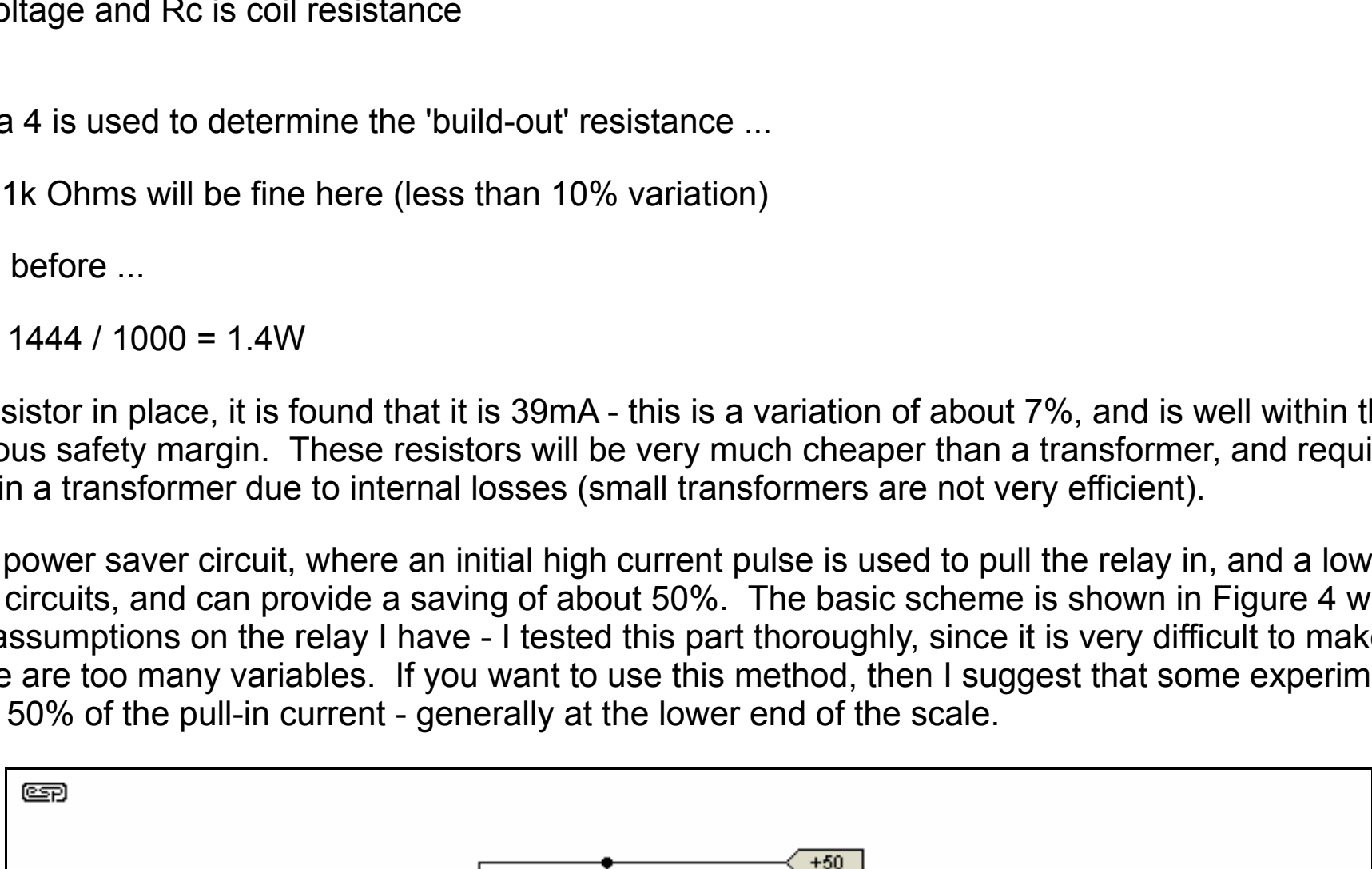


Figure 2 - Auxiliary Transformer Control Circuit

This is a simple bridge rectifier, and a small and adequate capacitor. The control circuit uses readily available and low cost components, and can easily be built on Veroboard or similar. All diodes can be 1N4004 or equivalent. Use a transformer with a 9V AC secondary, which will supply close enough to 12 Volts for this circuit. No regulation is needed, and the controller is a simple timer, activating the relay after about 100ms. I have chosen a MOSFET for the switch, since it has a defined turn-on voltage, and requires virtually no gate current. With the component values shown, the relay will activate in about 100 milli-seconds. This can be increased (or decreased) by increasing (decreasing) the value of R1 (27k). The transformer need only be a small one, since current is less than 100mA.

Note Carefully: The value shown for R1 (27k) may need to be varied to obtain the required time delay of around 100ms. The actual value needed depends on the switching threshold for the MOSFET and the value of C2, which is an electrolytic cap and they have a wide tolerance. In general, expect the value to be somewhere between 27k and 56k, but in some (rare) cases you may need more or less than the range given.

The MOSFET (Q2 - 2N7000) has a gate threshold voltage that is quoted as being between 0.8V to 3V, with 2.1V given as the 'typical' value. As a result, you will need to adjust the value of R1 to obtain the correct delay. You could use a 100k trimpot if you like - that should cover most eventualities. Feel free to use a 2N7000 or similar low power MOSFET if that low, the timer will only run for about 30ms, so R1 would need to be increased to about 82k. At the high end (3V), R1 needs to be reduced to about 22k for a 100ms delay. Note that the PCB version uses an amp capacitor, so the timing is very predictable.

Q1 is used to ensure that power is applied to the relay quickly. When a voltage of 0.65V is sensed across the relay, Q1 turns on, and instantly completes the charging of C2. Without the 'snap action', the circuit will be sluggish, and is not suited to some of the other variations below. Feel free to use a 2N7000 or similar low power MOSFET if that low, the timer will only run for about 30ms, so R1 would need to be increased to about 82k. At the high end (3V), R1 needs to be reduced to about 22k for a 100ms delay. Note that the PCB version uses an amp capacitor, so the timing is very predictable.

NOTE: C1 should be rated at a minimum of 50V to ensure that the ripple current rating is sufficient to prevent capacitor heating. Be warned that if the cap gets warm (or hot), then its reliability and longevity will be compromised.

It is possible to make the relay release much faster, but at the expense of circuit complexity. A simple logic system could ensure that the circuit was reset with a single AC cycle dropout, but this would be too fast for normal use, and quite unnecessary. C1 (marked with a 7) will have to be selected based on the relay. If the value is too small, the relay will chatter or at least buzz, and will probably overheat as well, due to eddy currents in the solid core used in DC relays. The capacitor should be selected based on the value that makes the relay quiet, but still releases quickly enough to prevent high inrush current if there is a momentary interruption to the mains supply. The value shown (470uF) will generally be suitable for most applications.

You might wish to consider using a mains switch with an additional set of contacts, so that the second set will short circuit the 12V supply when power is turned off. Make sure that the switch has appropriate ratings, and be sure to mark and insulate all connections. This is not really necessary though, and for a DIY project I'd have to say that it's not recommended because of the risk. Mixing mains and low voltages on the same switch is very dangerous.

Where it is not possible to use the transformer for any reason, then the circuit in Figure 3 can be used. This uses a resistor to drop the supply voltage for the relay, and has a simple zener diode regulator to supply the control circuit. The method of determining the resistor values and power for Rx and Ry is shown below.

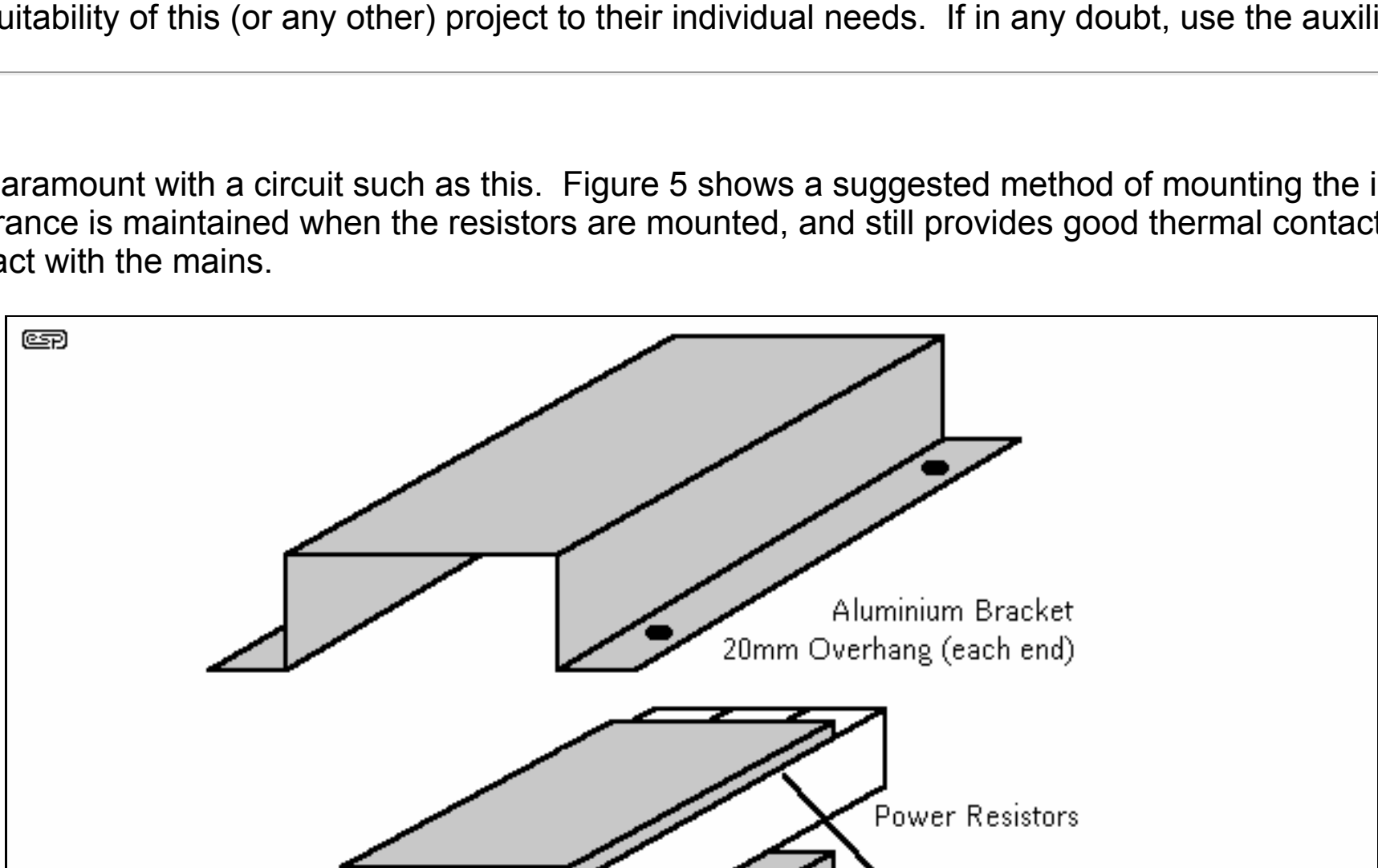


Figure 3 - Control Circuit Using Existing Supply

WARNING: In the event of an amplifier fault at power-on, the fuse may not blow immediately with this circuit installed, since there may be no power to operate the relay. The inrush is limited to 200% of that at normal full power, so the fuse may be safe for long enough for it to destroy the resistor(s)! The ballast resistors will overheat very quickly, and if you are lucky they will fail. If you don't like this idea - [Use The Auxiliary Transformer](#).

I very strongly suggest the auxiliary transformer - it is MUCH safer!

The first calculation is based on the supply voltage, and determines the current available to the zener. This should be about 20mA (it is not too much). Since the zener is 12V, use the following formula to obtain the value for Rx ...

$$R = (V_{cc} - 12) / I \quad (4) \text{ Where } V_{cc} \text{ is the voltage of the main positive supply rail, I is current}$$

Example. The Vcc (the +ve supply rail) is 50V, so ...

$$R = (50 - 12) / 0.02 = 1900 \text{ Ohms (1.8k is quite acceptable)}$$

Power may now be determined as follows ...

$$P = V_{cc} - 12 / R \quad (5) \\ P = (50 - 12) / 1900 = 38^2 / 1800 = 0.8W$$

A 2W resistor (or two 36V 1W resistors in parallel) is indicated to allow a safety margin. Where possible, I always recommend that a resistor be at least double the expected power dissipation, to ensure a long life and while construction is in progress. Commercial use is prohibited without express written authorisation from Rod Elliott.

The relay coil limiting resistor (Ry) is worked out in a similar manner, and first you have to know the resistance of the relay coil. This may be obtained from specifications, or measured with a multimeter. I have details of a suitable relay that has a 12V DC coil, and has a claimed resistance of 285 Ohms. Coil current is therefore ...

$$I = V_{cc} / R_c \quad (6) \text{ Where } V_{cc} \text{ is coil voltage and } R_c \text{ is coil resistance} \\ I = 12 / 285 = 0.042A (42mA)$$

Using the same supply as before, formula 4 is used to determine the 'build-out' resistance ...

$$R = (50 - 12) / 0.042 = 904 \text{ Ohms. 1k Ohms will be fine here (less than 10% variation)}$$

Power is determined using equation 5 as before ...

$$P = (50 - 12) / 1000 = 38^2 / 1000 = 1444 / 1000 = 1.4W$$

If the coil current is calculated with the resistor in place, it is found that it is 39mA - this is a variation of about 7%, and is well within the tolerance of a relay. A 5W resistor is indicated, as this has a more than generous safety margin. These resistors will be very much cheaper than a transformer, and require less space. Wasted power is not great, and is probably more than that lost in a transformer due to internal losses (small transformers are not very efficient).

With relays, it is often beneficial to use a power saver circuit, where an initial high current pulse is used to pull the relay in, and a lower holding current is then used to keep it energised. This is very common in relay circuits, and can provide a saving of about 50%. The basic scheme is shown in Figure 4 with some typical values for the relay as mentioned in the text. I have based my assumptions on the relay I have - I tested this thing thoroughly, since it is very difficult to make calculations based on an electro-mechanical device such as a relay - there are too many variables. If you want to use the relay, but this circuit (and the PCB) simplifies the construction process considerably. The relay holding current will generally be about 50% of the pull-in current - generally at the lower end of the scale.

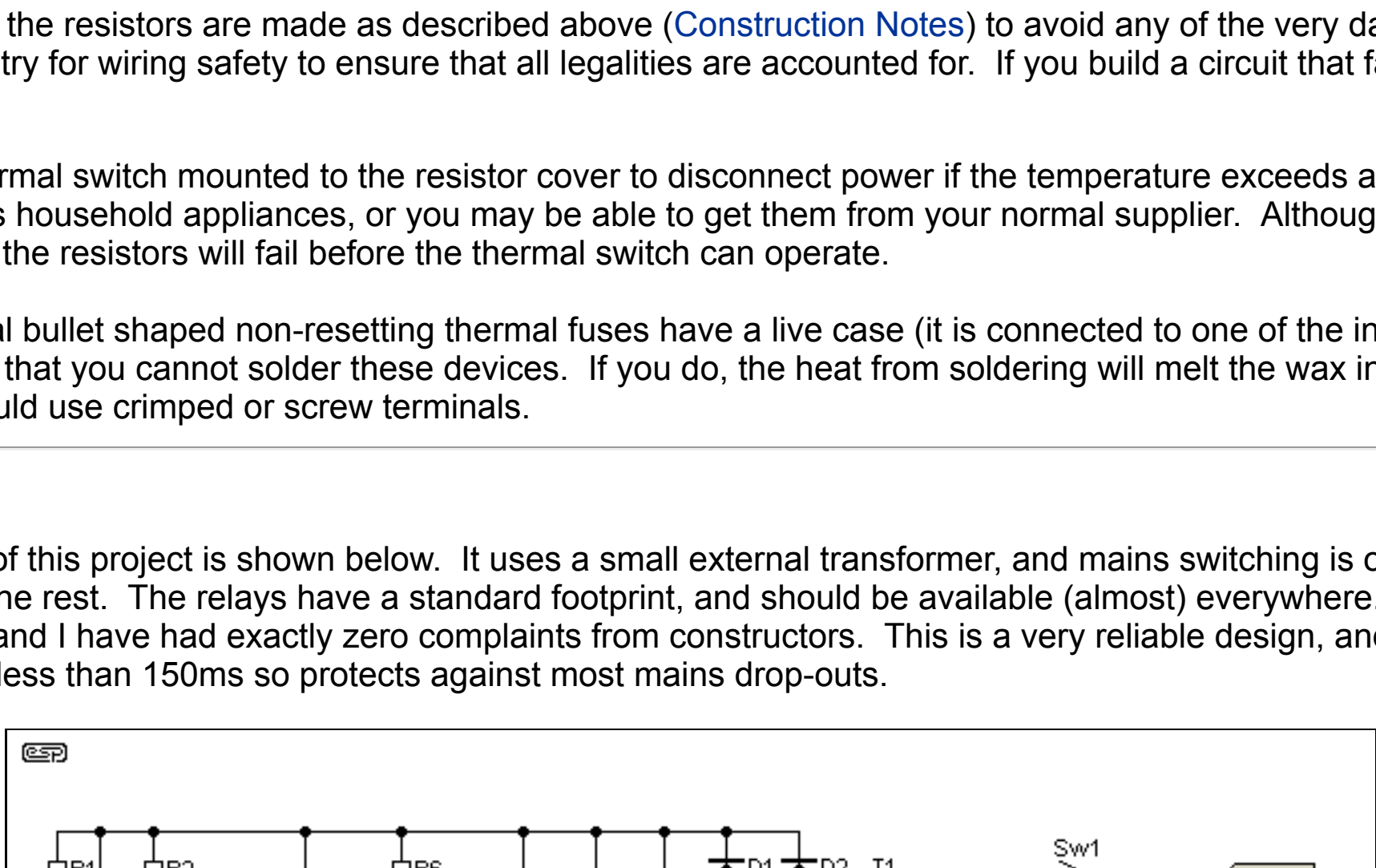


Figure 4 - Power Saving (Efficiency) Relay Circuit

The values shown for those estimated for the 12V, 285 Ohm relay - yours may be different! Do not mess about with this method if you are unsure of what you are doing. Failure of the relay to operate will cause the ballast resistors to overheat, with possibly catastrophic results (See below). This method can also be used with Class-A amps, as it is possible to make sure that the relay activates even on the lower voltage present while the ballast resistors are in circuit. (I strongly suggest the separate power supply circuit for Class-A, see [Class-A Amplifiers](#), below.)

Notice that the power savings are across the board. The very fast resistor now will dissipate 0.8W instead of 1.4W, and the auxiliary limiting resistor is now a 0.5W type - instantaneous dissipation is only 0.7W, and that is for a very short time. The feed resistor is now 2k2 instead of 1k, but an extra capacitor and resistor are the price you pay. The capacitor can be used in the circuit of Figure 3 too, and will force a large current at turn on. This will not save any power, but will most certainly ensure that the relay pulls in reliably.

A Few Test Results

The relay I suggest has a 44mA coil, so relay current is 44mA for each relay. Basic specifications are as follows ...

- Nominal current - 44mA
- Pull-in Current - 33mA
- Drop-out Current - 5mA

Most (all?) relays will hold in perfectly well at 1/2 rated current, and I would suggest that this is as low as you should go for reliability. If you don't feel like including it, the power that one 1N4004 may be made for reference while construction is in progress. Commercial use is prohibited without express written authorisation from Rod Elliott.

Make sure that the mains connections to the resistors are made as described above ([Construction Notes](#)) to avoid any of the very dangerous possibilities. You may need to consult the local regulations in your country for wiring safety to ensure that all legalities are accounted for. If you build a circuit that fails and kills someone, guess who is liable? You!

It is possible to use a thermal switch mounted to the resistor cover to disconnect power if the temperature exceeds a set limit. These devices are available as spare parts for various household appliances, or you may be able to get them from your normal supplier. Although this may appear to be a desirable option, it is probable that the resistors will fail before the thermal switch can operate.

WARNING: The small metal bullet shaped non-resetting thermal fuses have a live case (it is connected to one of the input leads). Use this type with great caution! Also, be aware that you cannot solder these devices. If you do, the heat from soldering will melt the wax inside the thermal fuse and it will be open circuit. Connections should use crimped or screw terminals.

PCB Version

The circuit diagram for the PCB version of this project is shown below. It uses a small external transformer, and almost everything is only required for the small transformer's secondary, and the circuit takes care of the rest. The relays have a standard footprint, and should be available (almost) everywhere. Hundreds of these have been built since the PCB was first offered for sale, and I have had exactly zero complaints from constructors. This is a very reliable design, and it does everything exactly as it should. The delay is predictable, and it resets in less than 15ms so protects against most mains drop-outs.

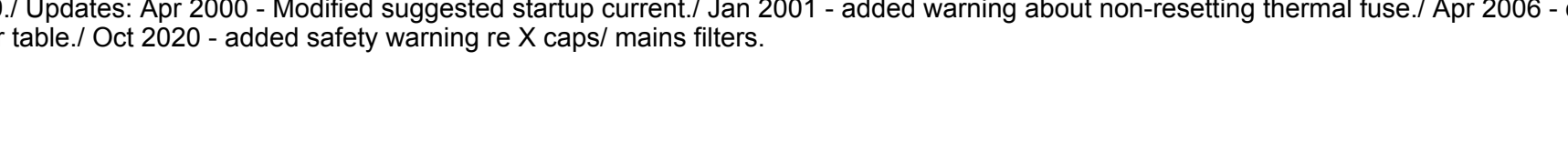


Figure 6 - PCB Version of Soft Start Mains Switch

A 9V transformer is needed, having a rating of